
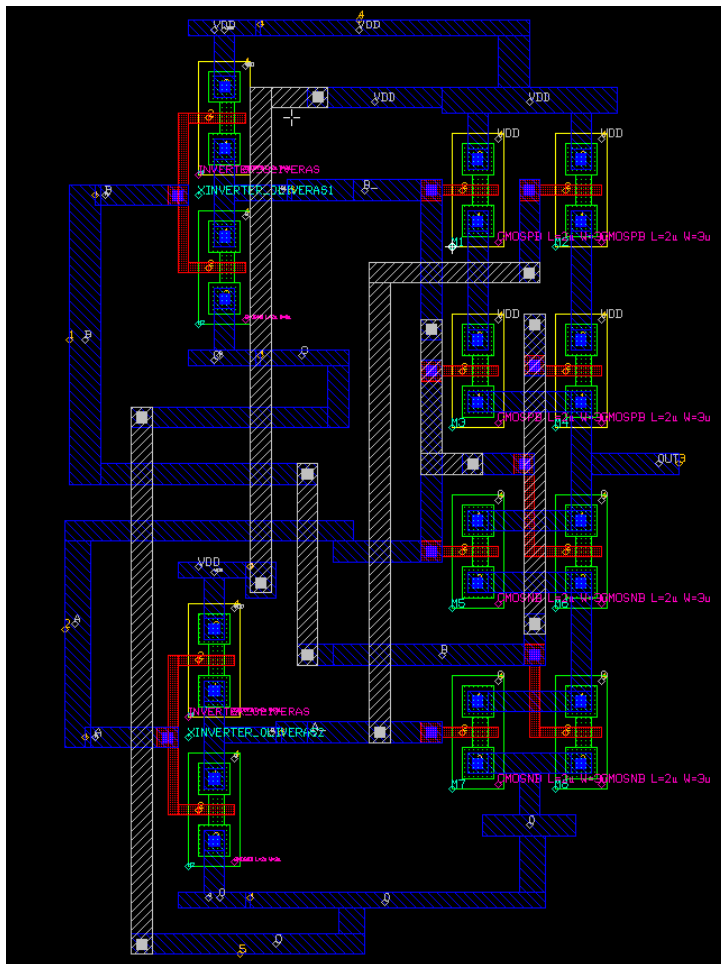


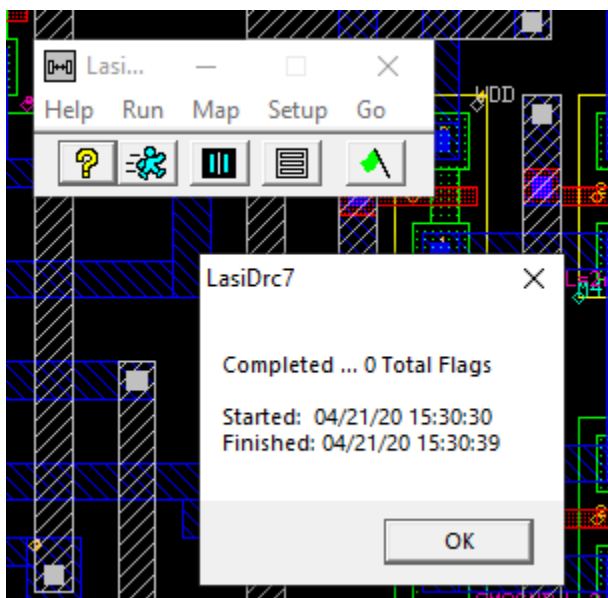
Assignment 3 (Lab 3) – XOR 2-Input Design




LASIDRC




LASICKT

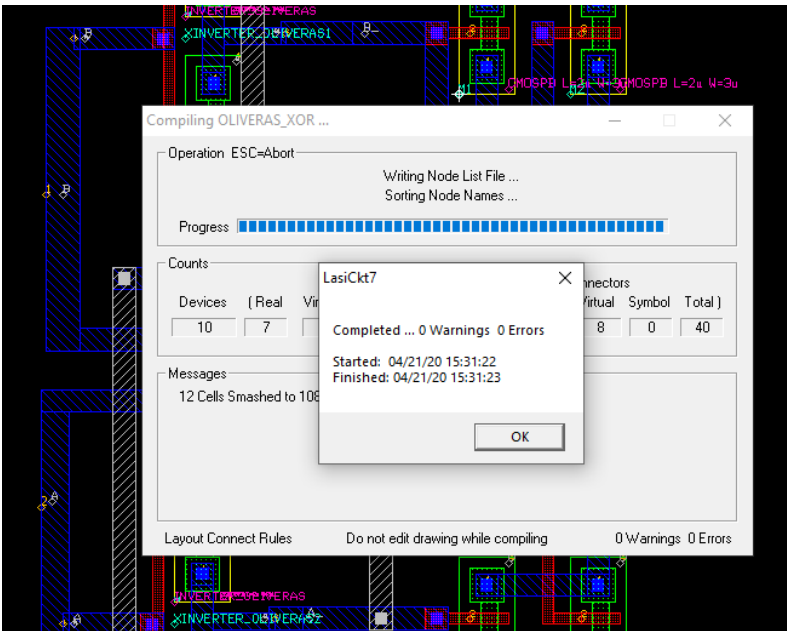


Waveforms

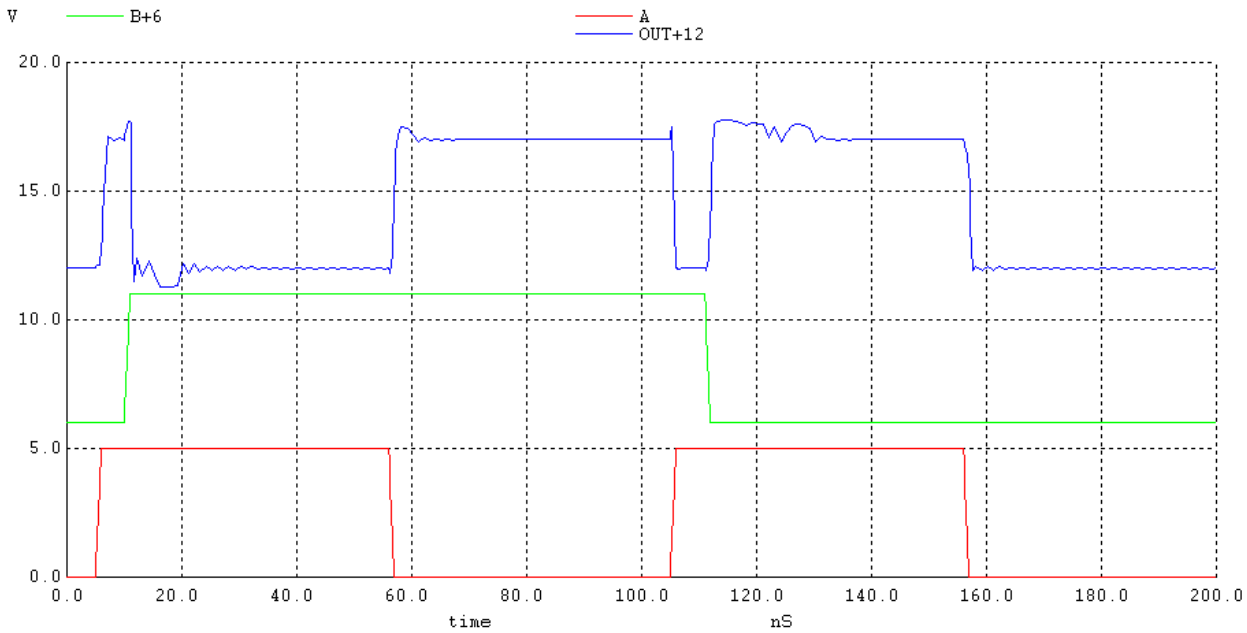


Half Adder Design

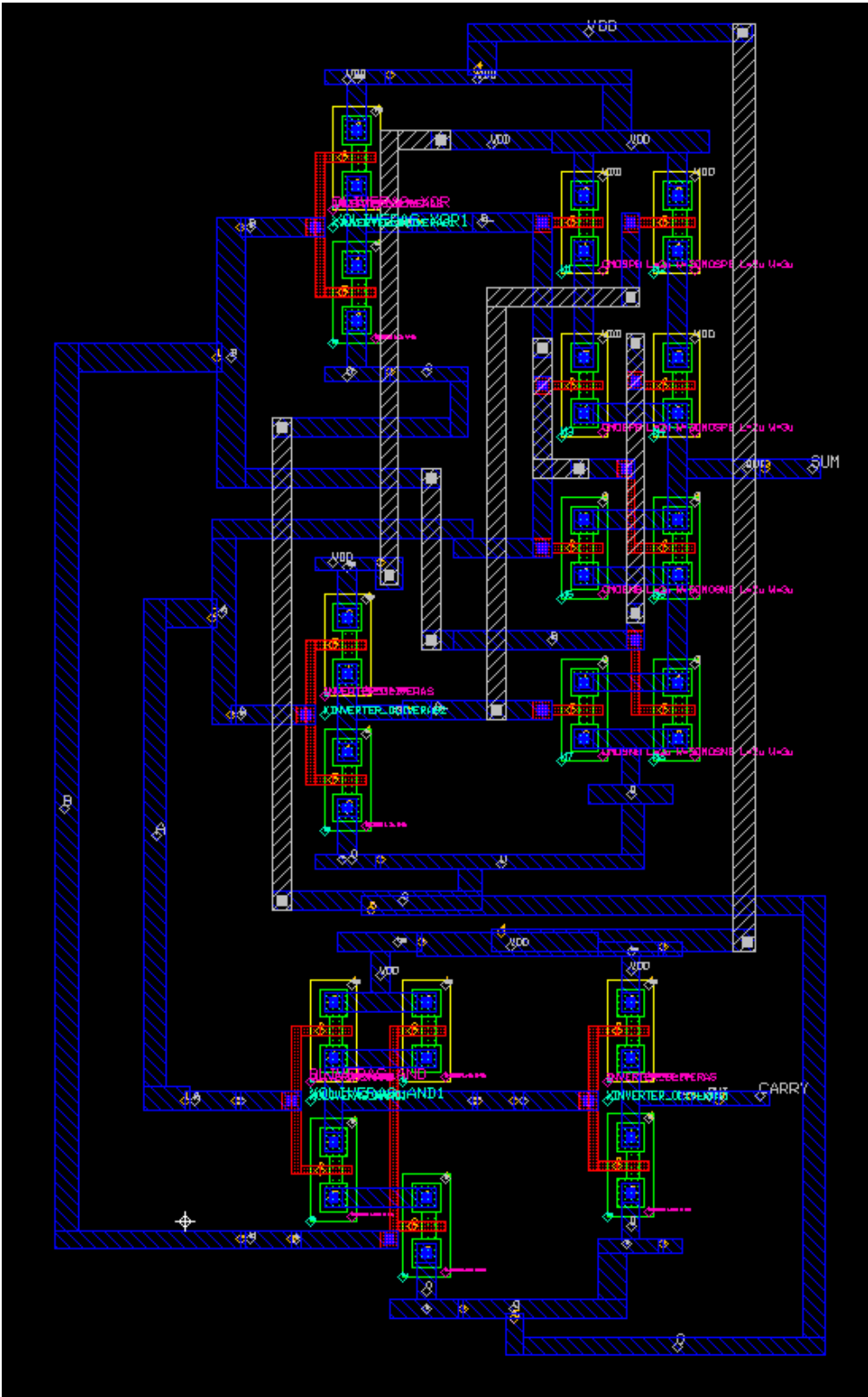

LASIDRC

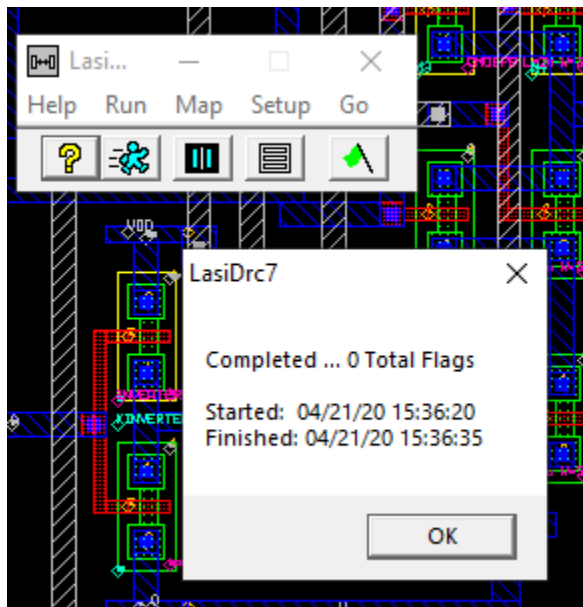

LASICKT

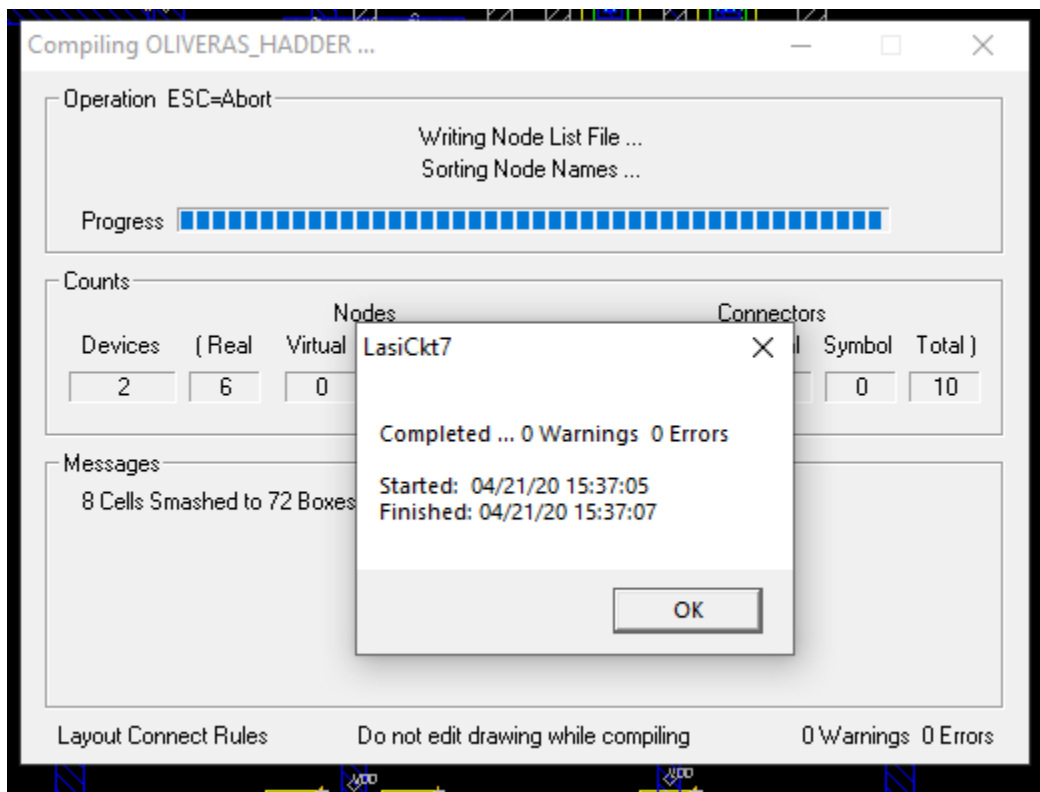

Waveforms

