

Ivan Oliveras:

1. Lab Assignment Pages

• CDA3201 • Intro to Logic Design •

Lab Assignment

1

Name: Ivan Oliveras

Z#: 23466359 Grade: /100

1. [100] To get your lab points you need to get your lab grader by the Teaching Assistnat (TA) and submit under Canvas > Assignment > Lab 1 a **portfolio** consisting of one pdf file that includes:


- your handwork in this lab,
- a capture of your schematic done in Quartus – must include comment with your name and Z#
- a capture of your waveform simulation done in Quartus for all 3 circuits resulting from lab 1
- a picture of your breadboard
- a picture of your gradesheet containing the grade and signature of TA

- 1.1 [10] Given the following Boolean Algebra Equation, complete the Truth Table

$$X = B\bar{C}\bar{D} + B\bar{C}D + A\bar{B}\bar{D} + AB\bar{C}\bar{D}$$

ABCD	$B\bar{C}\bar{D}$	$B\bar{C}D$	$A\bar{B}\bar{D}$	$AB\bar{C}\bar{D}$	X
0000	0	0	0	0	0
0001	0	0	0	0	0
0010	0	0	0	0	0
0011	0	0	0	0	0
0100	0	0	0	0	0
0101	0	0	0	0	0
0110	1	0	0	0	1
0111	0	1	0	0	1
1000	0	0	1	0	1
1001	0	0	0	0	0
1010	0	0	1	0	1
1011	0	0	0	0	0
1100	0	0	0	1	1
1101	0	0	0	0	0
1110	0	0	0	0	0
1111	0	1	0	0	1

 - 1.2 [10] Utilizing the NOT AND OR gates provided below, label the input that you need to put through NOT, determine how many inputs are needed for each gate and use the number of gates you need (there may be extras). Draw the circuit connections to implement X exactly as specified.



$$X = B\bar{C}\bar{D} + B\bar{C}D + A\bar{B}\bar{D} + AB\bar{C}\bar{D}$$

- 1.3 [10] Create a project in Altera Quartus called **lab1-PETRIE-yourlastname** following Dr. Petrie's step by step guide and verify the circuit you designed in 1.2 works according to 1.1 Truth Table. If it does not work as specified by the Truth Table, then determine if error is in the Truth Table or your design. Create with same name a Block Diagram/Schematics (.bdf) of your design in 1.3. Is there a 4-input OR gate available? If there is not then figure out how you will change the design using 2 input OR gates. Generate with same name a Waveform file (.vwf), group the inputs and set the counter to step through all the values, Compile, and Simulate. Make sure to save the project, the .bdf and .vwf files often. Check the .vwf to verify it produces same results as the Truth Table 1.1. Keep the project and files to expand the Block Diagram to include the other 2 circuits in the rest of lab 1.

Z#: 23466357 **Grade:** /100

Lab 1, page 2

Name: *Juan Ollerias*

Z#: *23966357* Grade: */100*


As you verified in 1.a.6, the following Boolean function is algebraically reduced to two different forms denoted as X1 and X2 as follows.

$$\begin{aligned} X &= BC\bar{D} + B\bar{C}D + A\bar{B}\bar{D} + A\bar{B}C\bar{D} \\ &= BC(\bar{D} + D) + (\bar{B} + B\bar{C})A\bar{D} \\ &= BC + (\bar{B} + \bar{C})A\bar{D} = \underline{BC + A\bar{B}\bar{D} + A\bar{C}\bar{D}} = X1 \\ \text{or } &= BC + (\bar{B}C)A\bar{D} = \underline{BC + A\bar{D}} = X2 \end{aligned}$$

ABCD	BC	A $\bar{B}\bar{D}$	A $\bar{C}\bar{D}$	A \bar{D}	X1	X2
0000	0	0	0	0	0	0
0001	0	0	0	0	0	0
0010	0	0	0	0	0	0
0011	0	0	0	0	0	0
0100	0	0	0	0	0	0
0101	0	0	0	0	0	0
0110	1	0	0	0	1	1
0111	1	0	0	0	1	1
1000	1	1	1	1	1	1
1001	1	1	1	1	1	1
1010	1	1	1	1	1	1
1011	1	1	1	1	1	1
1100	1	1	1	1	1	1
1101	1	1	1	1	1	1
1110	1	1	1	1	1	1
1111	1	1	1	1	1	1

1.7) [5] Verify the equivalence of X1 and X2 using the following truth table:

 1.8) [7] Design the circuit for the above two reduced functions, X1 and X2, using exactly 3 NOT gates, 4 2-input AND gates, 3 2-input OR gates. Note, there will not enough gates unless you are able to reuse by finding things both equations have in common.




1.9) [10] Verify the circuit design/behavior by implementing the circuit using Quartus before you actually build the circuit on the breadboard. Open the Quartus project you build in 1.a.3 and add the X1 and X2 circuits to the X circuit Block Diagram / Schematics. Add the X1 and X2 inputs to the Waveform File and Compile and Simulate, check if all $X = X_1 = X_2$. You will show the TA you have these files and submit the .bdf and .vwf to the Lab 1 together with the scan of this completed Lab with all your work. Dr. Petrie will adjust your grade – these 2 points will be converted to 20 points total for this section and 1.a.3.

Name: *Ivalli Oliveras*

Z#: *23466358* Grade: */100*

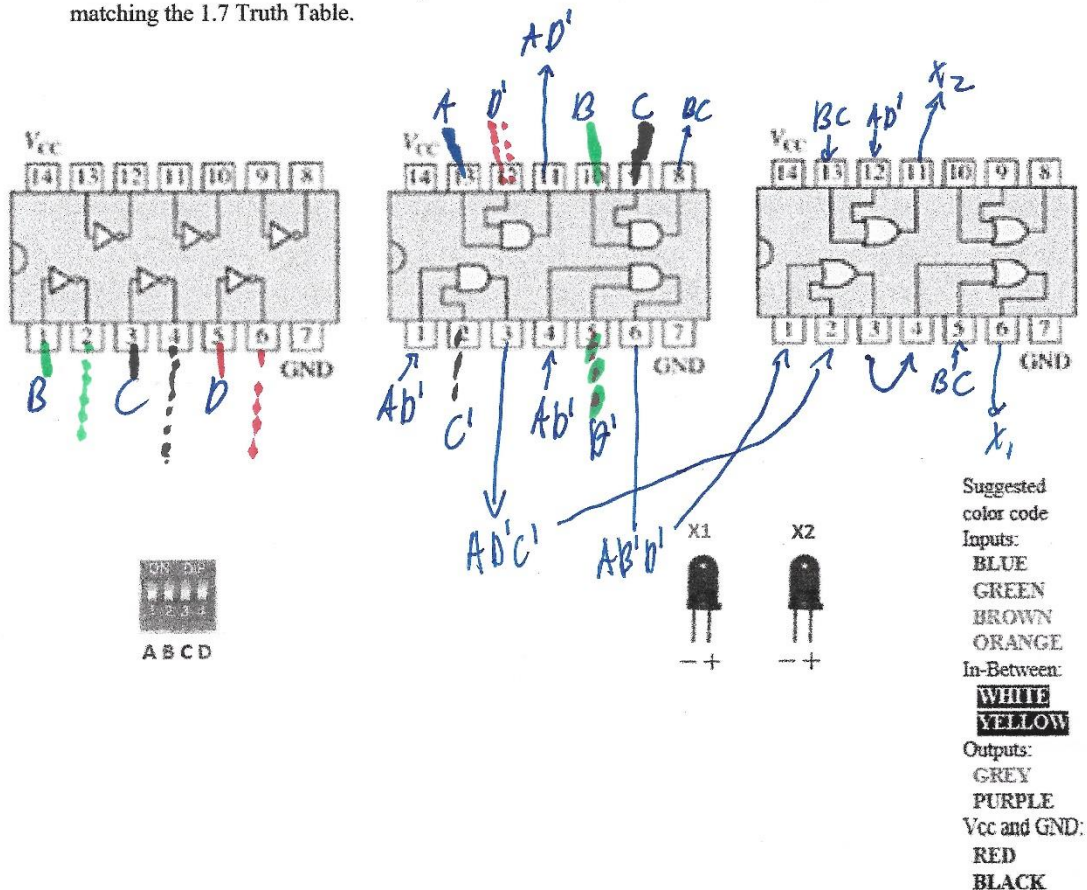
1.10) [20] Use the following chip pin-out to conveniently plan your wiring to build the above 2-output circuit for X1 and X2 on your breadboard using exactly 1/2 7404, 1 7408 and 3/4 7432 chips on your breadboard and then connect inputs ABCD to 4 DIP switched and the outputs X1 X2 to two LED indicators. Test all the 16 different input combinations and observe the two outputs to be equivalent and matching the 1.7 Truth Table.




After you get it to work but before the TA grades it, take a picture of your breadboard to submit as part of Lab 1 documentation. After it is graded take a picture of the gradesheet, then, except for the ground and power wires, pull the wires attached to the three the three ICs on the upper breadboard you used for this experiment (Do NOT pull the lab platform wires just the ones in the upper breadboard), leaving the three ICs plugged into your board with power and ground connected. **KEEP THE WIRE TO REUSE FOR NEXT LAB.** Upload the portfolio of your labwork to Canvas to validate your lab grade.

The top screenshot shows a logic circuit diagram for a 4-input function. The inputs are A, B, C, and D, each connected to a switch labeled 'INPUT VCC'. The circuit implements the function $X = BCD + BCD + AB'D + ABC'D$. The logic consists of four 3-input AND gates (inst1, inst2, inst3, inst4) and one 4-input OR gate (inst9). The output is X. The bottom screenshot shows a logic circuit diagram for a 4-input function. The inputs are A1, B1, C1, and D1, each connected to a switch labeled 'INPUT VCC'. The circuit implements the functions $X1 = BC + AB'D + AC'D$ and $X2 = BC + AD$. The logic consists of four 2-input AND gates (inst14, inst15, inst16, inst17), two 2-input OR gates (inst23, inst24), and two 2-input NOT gates (inst19, inst20, inst21). The outputs are X1 and X2. The bottom screenshot also includes a timing diagram showing the waveforms for inputs A, B, C, D, X1, and X2 over a time range from 0 to 390 ns. The timing diagram shows that the circuit correctly implements the specified functions.

Graded Circuit and Proof

 

 

Name: Ivan Oliveras Z# 23466357 X

000-75095

CERTIFICATE
000-75095

000-75095

Logic Lab Grading Rubric

Lab#	Title	Time (hrs)	Bench	Pre-Work	Quizzes	Schematic	Wiring Diagram	Used Breadboard Wires	Working	Bonus	Cleaned up	Score (100%)	Date & Time	TA Name & Initials
0	Infrastructure & Setup: The breadboard & logic probe	1												
1	Boolean Algebra & Quizzes	1	43	43	50%	25% for Logic Gates only	10%	5%	10%	10%	10%	10%	9/19/2016	Umar Al-Azzak
2	adder	2												
3	Decoder: Implementation of 7490 Display	2												
4	Flip-Flop #1	2												
5	Flip-Flop #2	2												
6	2 Decade Counter & Hex	2												

