


- 0) [5] This lab experiment is used for the lab orientation where TAs will walk you through practical steps to build the experiment circuit and test it. You will use the following simple function:

$$Z = A'B + AC$$

- 0.a) [0] Fill the truth table for the above function

ABC	A'B	AC	Z
000	0	0	0
001	0	0	0
010	1	0	1
011	1	0	1
100	0	0	0
101	0	1	1
110	0	0	0
111	0	1	1

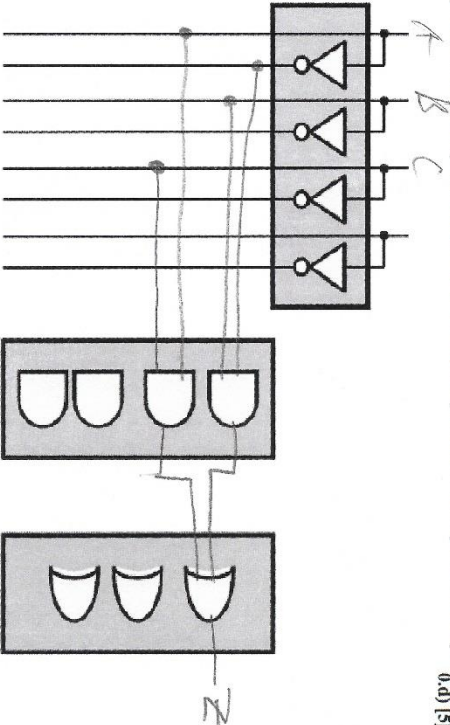
- 0.b) [0] Draw the switching function ( $Z = A'B + AC$ ) using Inverters, AND gates, and OR gate



- 0.c) [0] Using the three logic chips below, draw the wires to make the needed connections between the various gates. Note that not all gates in all chips are used.

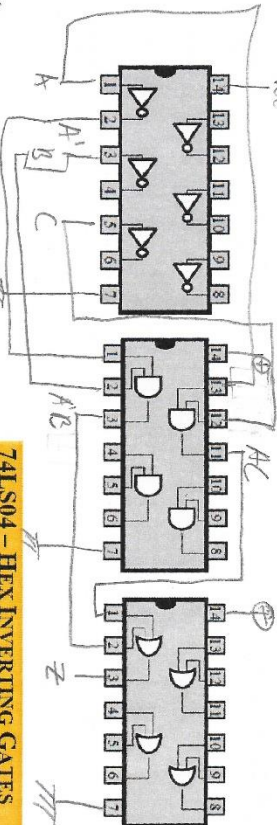- 0.d) [0] Using the three logic chips below, draw the wires to make the needed connections between the various gates. Note that not all gates in all chips are used.

*NOTE FROM DR. PETRIE – Do not remove NOT, AND, OR, and NAND chips and wires from 1<sup>st</sup> port. Look at gates that you did not use in those chips, identify the switches that you will designate A, B, C, note you already have available A and A'. Utilize the open gates and draw the circuits for  $Z = A'B + AC$*



- 0.d) [5] With the wiring diagram above, you are ready to implement the circuit on the breadboard.

For inputs ABC, use three DIP switches (most left) with all in off position (ABC = logic 000).

*Note from Dr. Petrie: Decide which bank of switches you want to use or reuse the inputs you had before.*

For output Z, use one of the LED indicators (most right). If output Z is logic 1, the LED should be on. Note that all switches and LED indicators are active high.

Next use the 3 DIP switches to try all binary combinations of inputs ABC and observe the output Z if it turns on and off according to the truth table above. If you have a perfect match, it means you wired the circuit correctly, and you completed lab 0.

To check the logic level of any pin on any chip, use the probe wire

### 74LS04 - HEX INVERTING GATES

Connection Diagram

Function Table

Input	Output
0	1
1	0

### 74LS08 - QUAD 2-INPUT AND

Connection Diagram

Function Table



Input	Output
0	0
1	1

### 74LS32 - QUAD 2-INPUT OR

Connection Diagram

Function Table

Input	Output
0	0
1	1

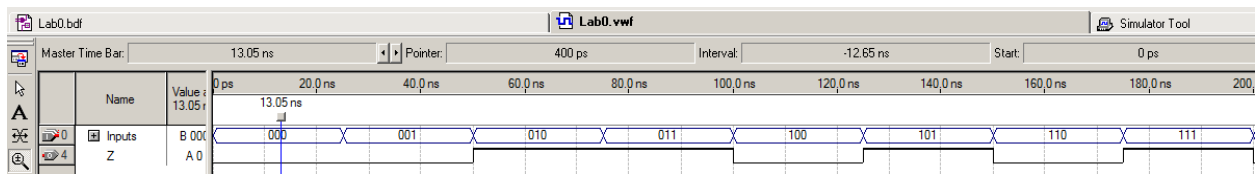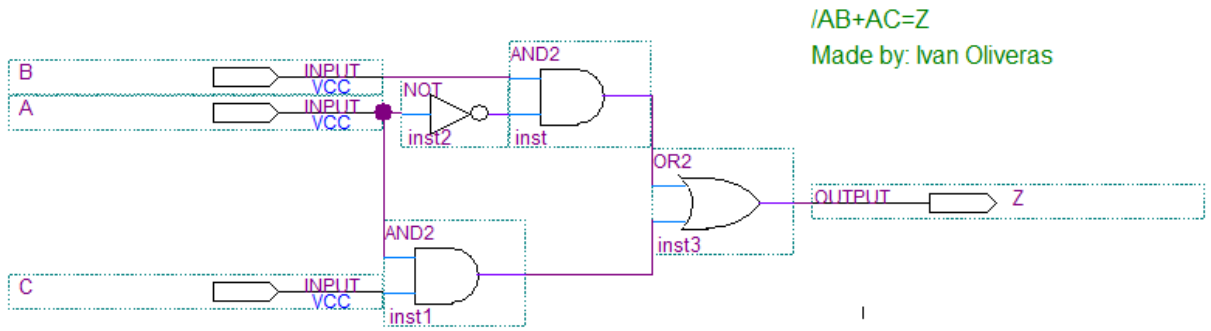




Name: Ivan Oliveras

000-75095

**CERTIFICATE OF AUTHENTICITY**

ISSUED TO: 000-75095

DO NOT REMOVE OR TAMPER WITH

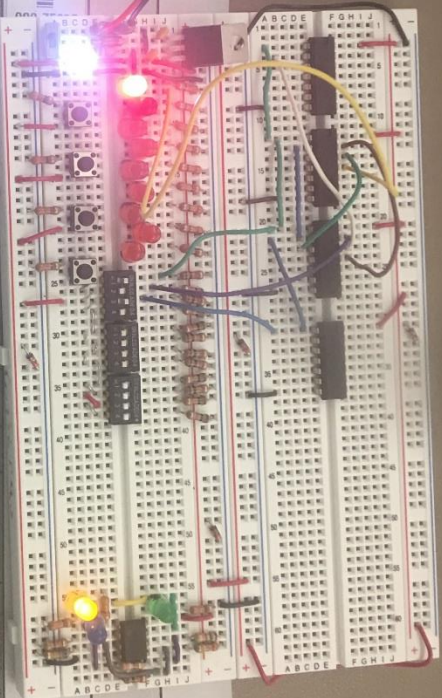

Lab#	Title	Time (hrs)	Bench#	Pre-Work	Quizzes	Schematic	Writing Diagram	Used Many Wires	Working	Bonus	Cleaned up	Score (100%)	Date & Time	TA Name & Initials
0	Introduction & Demo: Hardware & Software	1						10% Bonus: 10% (100% only)	10%	10%	10%	100%	01/22/2019	Ivan F. Oliveras
1	Boolean Simplification & Quizzes	1												
2	Adder - NAND	2												
3	Decoder: 1 Segment of 7-seg. display	2												
4	Flip-Flop #1	2												
5	Flip-Flop #2	2												
6	2 Digit Counter 2 Decade Counters & Mux	2												

FLORIDA ATLANTIC UNIVERSITY

**OWL CARD**

Anak Wannaphasachayong

Issued: 08/24/2016

Student

A21976005528423A

FLORIDA ATLANTIC UNIVERSITY

**OWL CARD**

Ivan F. Oliveras Diaz

Issued: 01/18/2018

Student

A21976006061408A